

RL CIRCUITS


EARLIER WE CONSIDERED A BASIC, YET IMPORTANT, ELECTRICAL CIRCUIT THAT EXHIBITED A TIME-DEPENDENT CURRENT, THE RC CIRCUIT.

GIVEN THE ANALOGIES BETWEEN INDUCTORS AND CAPACITORS, ONE MIGHT SUSPECT THAT WE COULD FORM AN ANALOGOUS CIRCUIT FROM A RESISTOR AND INDUCTOR.

A CIRCUIT THAT CONSISTS OF A RESISTOR, INDUCTOR, AND PERHAPS A BATTERY IS CALLED AN RL CIRCUIT.

DRAWING #2: RL CIRCUITS 2


CONSIDER THE FOLLOWING RL CIRCUIT:

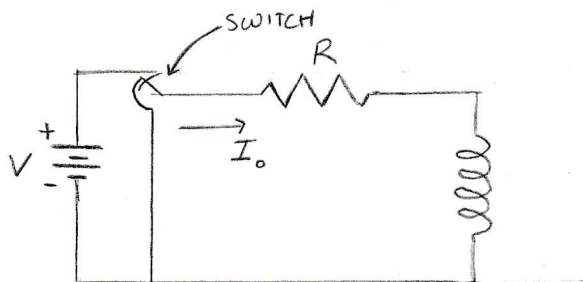

UP TO TIME $t = t_0$:

- ASSUME THAT THE SWITCH HAS BEEN IN THE UP POSITION FOR A LONG TIME
- ... THEN I_0 IS STEADY (i.e., $dI/dt = 0$) ...
- ... WHICH MEANS THAT THERE IS NO POTENTIAL DIFFERENCE ACROSS THE INDUCTOR ...
- ... AND THEREFORE THE CURRENT IN THE CIRCUIT IS DETERMINED ENTIRELY BY THE BATTERY AND RESISTOR ($I_0 = V/R$).

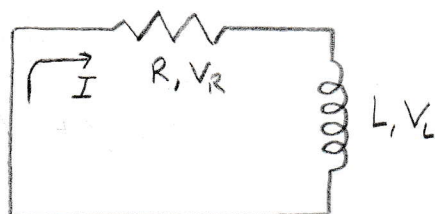SUPPOSE THAT AT $t = t_0$ THE SWITCH IS MOVED TO THE DOWN POSITION, THE CIRCUIT THEN LOOKS LIKE:



NOTE: THE CURRENT DOES NOT STOP IMMEDIATELY.

ACCORDING TO THE KIRCHHOFF LOOP LAW:

$$V_R + V_L = 0$$

$$-IR - L \frac{dI}{dt} = 0$$

$$\left(V_R = -IR, V_L = -L \frac{dI}{dt} \right)$$

(NOTE: THE MINUS SIGN IN V_R

ARISES BECAUSE THERE IS

A VOLTAGE DROP ACROSS

THE RESISTOR, IN THE

DIRECTION OF THE CURRENT)

DRAWING #3: RL CIRCUITS 3

REARRANGING THE PRIOR EXPRESSION:

$$-IR - L \frac{dI}{dt} = 0$$

$$-L \frac{dI}{dt} = IR$$

$$\frac{dI}{dt} = -I \frac{R}{L}$$

$$\frac{1}{I} dI = -\frac{R}{L} dt$$

$$\frac{1}{I} dI = -\frac{1}{(L/R)} dt$$

THE CURRENT AS A FUNCTION OF TIME CAN BE FOUND BY INTEGRATING THE PRIOR EXPRESSION:

$$\int_{I_0}^I \frac{dI}{I} = \int_{t_0}^t dt \left(-\frac{1}{(L/R)} \right) \quad (\text{NOTE THE LIMITS OF INTEGRATION})$$

$$\int_{I_0}^I \frac{dI}{I} = -\frac{1}{(L/R)} \int_{t_0}^t dt$$

$$\ln I \Big|_{I_0}^I = -\frac{1}{(L/R)} t \Big|_{t_0}^t$$

$$\ln I - \ln I_0 = -\frac{1}{(L/R)} (t - t_0)$$

$$\ln \left(\frac{I}{I_0} \right) = -\frac{1}{(L/R)} (t - t_0)$$

$$\frac{I}{I_0} = e^{-(t-t_0)/(L/R)}$$

$$I = I_0 e^{-(t-t_0)/(L/R)}$$

DRAWING #4: RL CIRCUITS 4

SINCE THE ARGUMENT OF THE EXPONENT MUST BE DIMENSIONLESS, (L/R) MUST HAVE DIMENSIONS OF TIME. WE CAN DEFINE THIS AS THE TIME CONSTANT τ OF THE RL CIRCUIT:

$$\tau = (L/R)$$

IN TERMS OF τ , WE CAN WRITE THE CURRENT IN THE RL CIRCUIT AS:

$$I = I_0 e^{-(t-t_0)/\tau}$$


EXPRESSIONS FOR V_R AND V_L CAN BE DERIVED ANALOGOUSLY TO THE WAY V_R WAS DERIVED FOR AN RC CIRCUIT.

→
DRAWING #4,1

IT CAN BE SEEN THAT THE CURRENT AS A FUNCTION OF TIME BEHAVES THE SAME AS IN AN RC CIRCUIT (THE EQUATIONS ARE THE SAME).

NOTE: WE MIGHT HAVE EXPECTED THIS, GIVEN THE SIMILARITIES BETWEEN CAPACITORS AND INDUCTORS.

GRAPHICALLY:

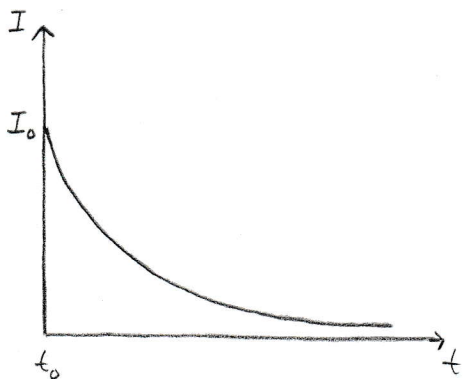

NOTE: IN PRACTICE, CAPACITORS (RC CIRCUITS) ARE USUALLY PREFERRED TO INDUCTORS (RL CIRCUITS), SINCE THEY CAN BE MORE EASILY MANUFACTURED AND ARE GENERALLY PHYSICALLY SMALLER.

DRAWING #4.1: THE TIME CONSTANT OF AN RC(RL) CIRCUIT

THE TIME CONSTANT OF AN RC(RL) CIRCUIT IS A USEFUL WAY TO CHARACTERIZE THE TIME-DEPENDENCE OF THE CURRENT (OR OTHER QUANTITY):

- AFTER τ , I WILL HAVE DECREASED TO $e^{-1}I_0$.
- AFTER 2τ , " " $e^{-2}I_0$.
- ... AND SO ON